

# ENGG 225

## Fundamentals of Electrical Circuits and Machines

Andy Smit

Winter 2019

### 1 Introduction

#### 1.1 Electric Circuits:

The interconnection of circuit elements in a closed path by conductors. The concept of electrical charge is the basics for describing all electrical phenomena. Charge exists in discrete quantities of integer multiples of  $1.60 \times 10^{-19}C$ . In circuit analysis there are two fundamental electrical quantities voltage and current.

#### 1.2 Electical Current:

Electrical current is defined as the rate of flow of electrical charges.


$$i(t) = \frac{dq(t)}{dt}$$

It is assumed that  $i$  is a measure of the equivalent flow of positive charge flow. Given  $i(t)$ , we can also find  $q(t)$


$$q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$

Normally there is an assigned reference direction for current. Often the direction is unknown and is assumed. The actual direction is determined by the sign of  $i$
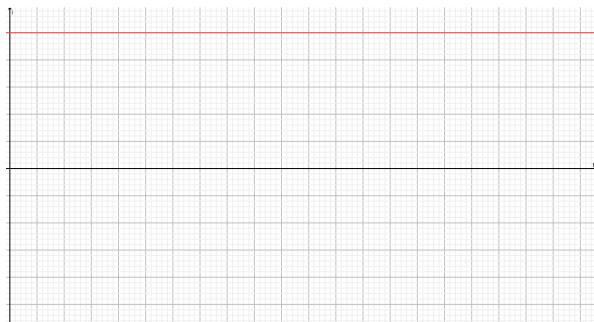
##### 1.2.1 Direct and Alternating Current:




(a) Direct Current

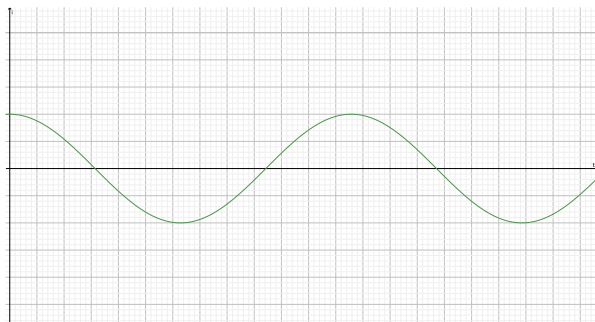

(b) Alternating Current

##### 1.2.2 Notation for Current in Circuit Diagrams

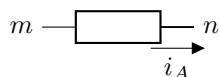

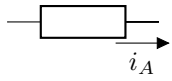


Figure 2: Branch Current

- 2 Resistive Circuits**
- 3 Operational Amplifiers**
- 4 Capacitors and Inductors**
- 5 Sinusoidal Currents and Voltages**